
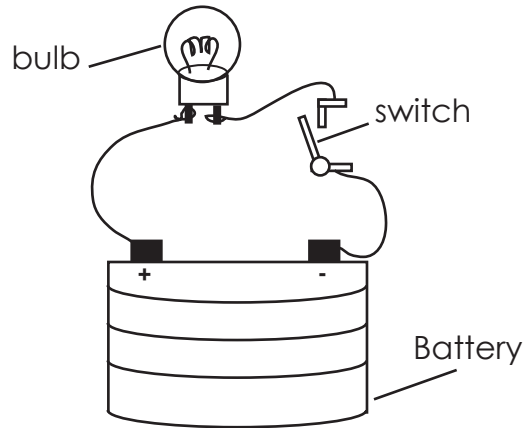


Name: _____ Class: _____

Electrical Circuits

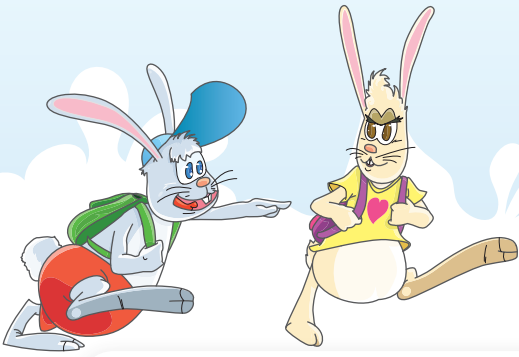


1. In the diagram above, is the bulb shining ? yes No
2. What must you do to turn on the bulb ?
 - a. detach the bulb from the cable
 - b. the switch should be closed
 - c. the switch should be open
 - d. tighten the ends of the battery
3. Electricity travels through a _____.
 - a. insulator
 - b. fire
 - c. switch
 - d. coil
4. _____ is a good conductor of electricity.
 - a. Copper
 - b. Cloth
 - c. Paper
 - d. Ceramic
5. What causes paper to stick to a pen that has been rubbed with a cloth ?
 - a. hydroelectricity
 - b. gum
 - c. static electricity
 - d. switching on and off
6. What is used to break an electric circuit ?
 - a. battery
 - b. a switch
 - c. a coil
 - d. a bulb



Name: _____ Class: _____

Electrical Circuits

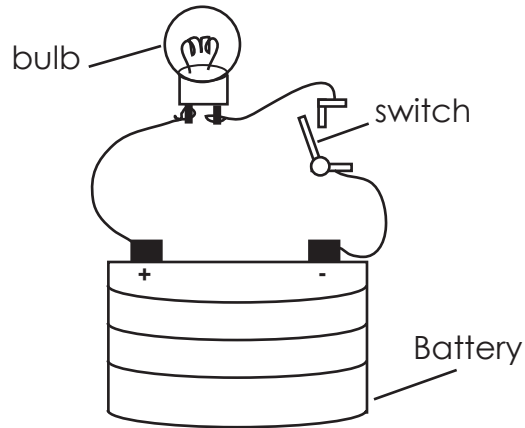

1. In the diagram above, is the bulb shining ? yes No
2. What must you do to turn on the bulb ?
 - a. detach the bulb from the cable
 - b. **the switch should be closed**
 - c. the switch should be open
 - d. tighten the ends of the battery
3. Electricity travels through a _____.
 - a. insulator
 - b. fire
 - c. switch
 - d. **coil**
4. _____ is a good conductor of electricity.
 - a. **Copper**
 - b. Cloth
 - c. Paper
 - d. Ceramic
5. What causes paper to stick to a pen that has been rubbed with a cloth ?
 - a. hydroelectricity
 - b. gum
 - c. **static electricity**
 - d. switching on and off
6. What is used to break an electric circuit ?
 - a. battery
 - b. **a switch**
 - c. a coil
 - d. a bulb